

ELECTRONICS:Color coding/Resistance Coding :-


$$R = 5600 \Omega \pm 10\%$$

* 1st strip = digit

* 2nd strip = digit

* 3rd strip = no. of zeros

* 4th strip = tolerance/inaccuracy/uncertainty (regarding the resistance you've found)

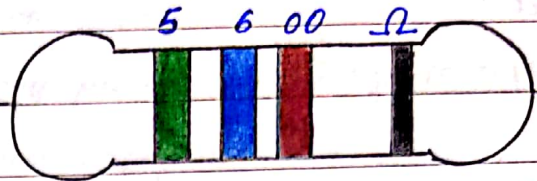

Black 0

→ start reading from right hand side

Brown 1

→ the list is given in the paper

Red 2

→ the last strip is on the extreme right of

Orange 3

the resistor, silver or golden in color

Yellow 4

↳ silver = 10%

iska matlab hai 10% ya 5%
ziada ya kam hoga uske val

Green 5

↳ gold = 5%

resistance compared to what you've found

Blue 6

** the power rating of a resistor is the maximum rate

Violet 7

of dissipation of electrical energy as heat before it

Grey 8

is damaged (0.25W to 1W is normally suitable)

White 9

POTENTIAL DIVIDER CIRCUIT:

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V$$

$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) V$$

Q. $R_1 = 3\Omega$ $R_2 = 6\Omega$ $V = 9V$

$$V_1 = \left(\frac{3}{3+6} \right) \times 9$$

$$V_2 = \left(\frac{2}{3+6} \right) \times 9$$

$$V_1 = \left(\frac{3}{9} \right) \times 9 = 3V$$

$$V_2 = \left(\frac{2 \times 9}{9} \right) = \frac{18}{5} V$$




Date: 10/9/20


e.g/ CD player

Potentiometer:

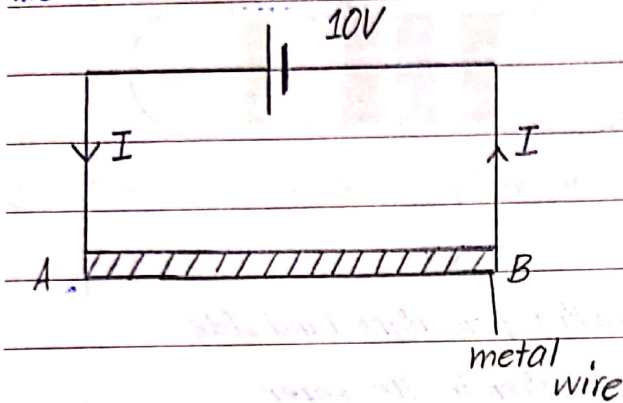- a type of variable potential divider
- an arrangement which is used to get variable voltage from the emf of the cell



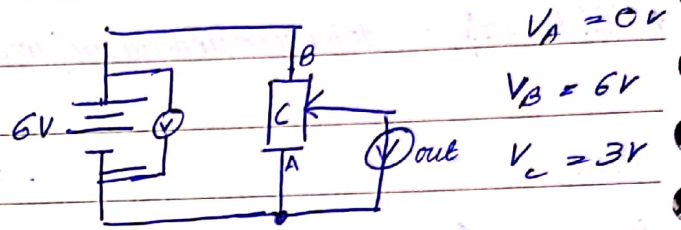*current is same for all points but resistance is not



Q. Find potential difference on any 2 points on the wire.

A. $V = IR$


$$V = I \left(\frac{\rho L}{A} \right)$$

$$V = \left(\frac{I \rho}{A} \right) L$$

*junction is a point in a circuit with a specific energy - two terminals of voltmeter connected to same junctions will give 0 voltage

$$V \propto \left(\frac{I \rho}{A} \right) L$$

$$V \propto L$$

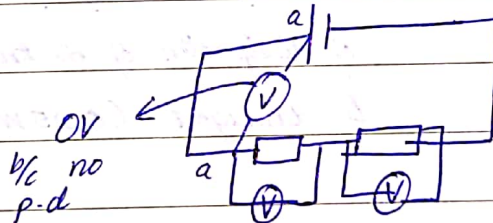


This means, potential difference across whole length is 10V, half length 5V and so on.

*if components are operated beyond their power ratings, they will overheat and will damage



Date: 10/9/20

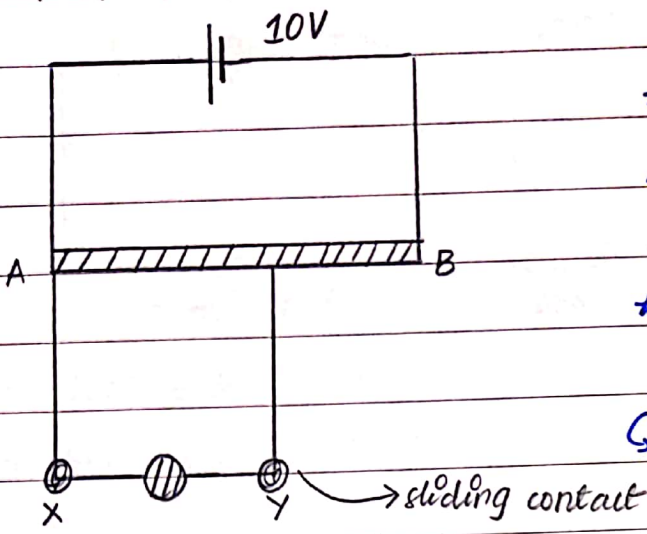

* as we move Y towards B through the sliding contact the voltage and speed increase

* aqay pechay kartay hain to voltage aur speed change hoti hai

↳ 0 pay lay aain gay tou fan band hojaye ga

→ intensity is being controlled

→ the dimmer is used to have this effect

$$R = \left(\frac{\rho}{A} \right) L$$

↳ jir side pay length ziada hain wahan pay resistance kam hogi


→ same cell provides variable voltage

Relay:

→ a device which is separated on small current and is used to automatically switch on and switch off another device which operates on large current

→ relay itself is on electromagnet


→ symbol

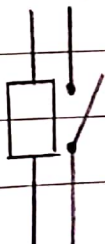

(a switch & a resistor)



Date: 11/9/20

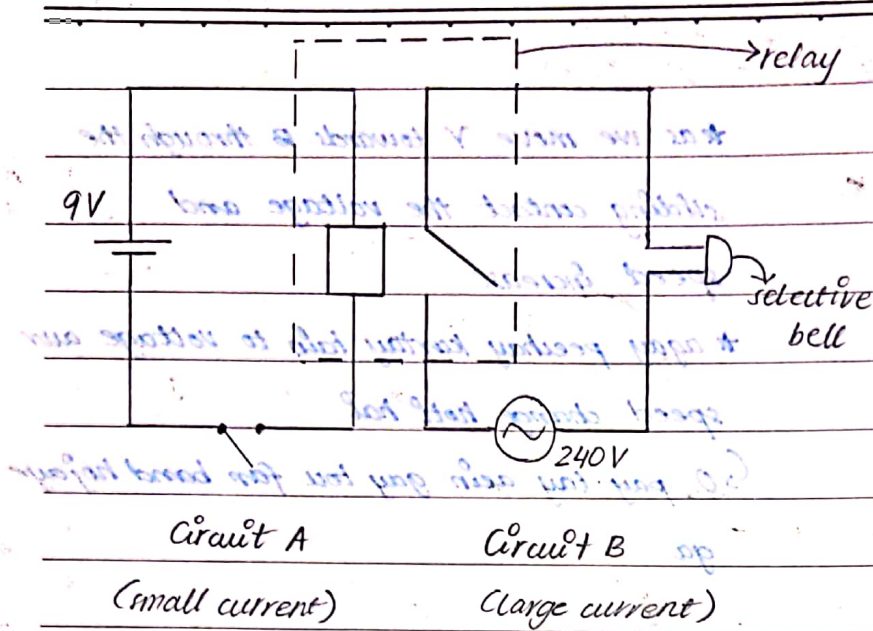

→ since the switch in circuit A is open, no current passes through relay.

↳ it won't become an electromagnet

↳ & won't be able to close second switch B

→ when the switch is closed, current passes through relay.

↳ it becomes an electromagnet

↳ as a result closes switch B

↳ & the selective bell rings

* When you press the doorbell you press the switch

Diode

→ a device which allows the current to flow in one direction only is called a diode


→ it converts alternating current to direct current

↳ process is known as rectification




02/09/21

Date: 11/9/20

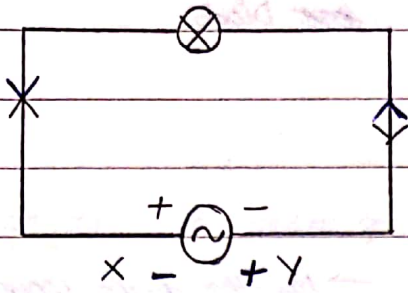


A.C : magnitude varies (0-7 A) ^{fluctuates from}
 D.C : magnitude same (7A throughout)

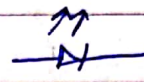*  : LED (light emitting diode) will only blink if A.C is being provided
 ↳ will glow if D.C

- +ve half cycle : X to Y
- -ve half cycle : Y to X

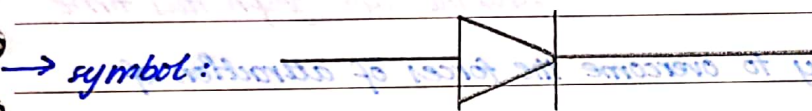
→ the diode conducts only positive cycles of A.C and does not allow the negative cycles to pass through it.




- * arrowhead represents direction of current
- * straight line will block current coming from the other end

Rectification:

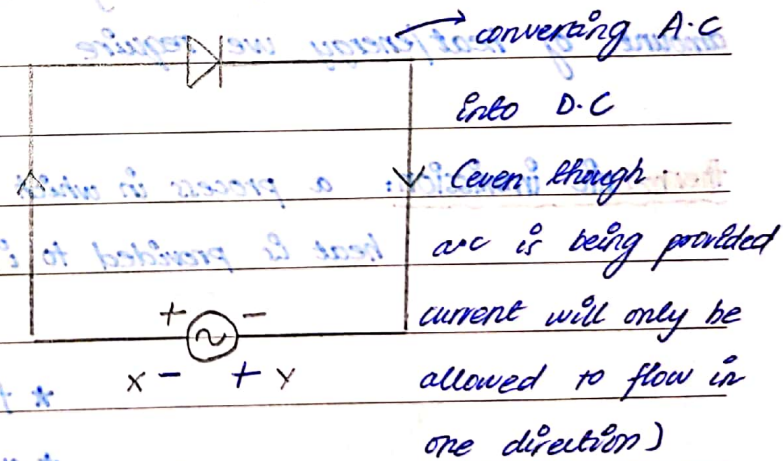
- +ve cycle kaylie current flow
- -ve kaylie nahin karnay dayga



A.C graph


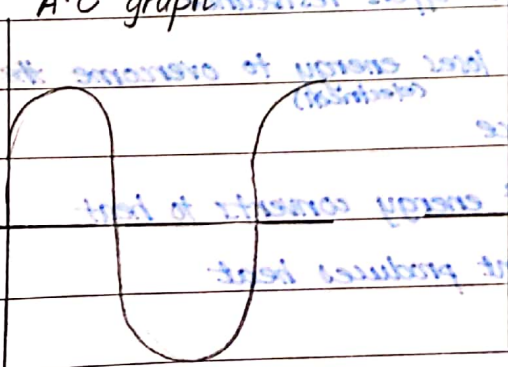


Diode graph (+ve only) (block -ve cycle)

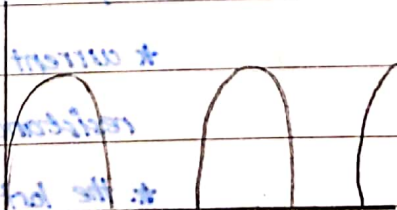

oc/p/11

Date: 15/9/20

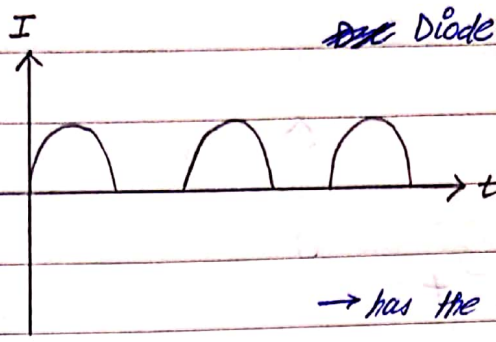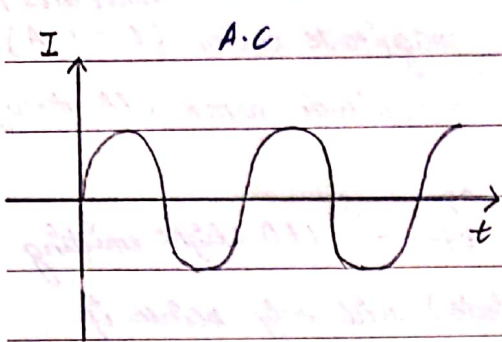

→ has the diode converted

Q. Are both of them A.C.?

A.C. to D.C.?

A. jir kay 2 axis hon woh A.C hota hai.


A. Yes but has only

changed direction not

magnitude which is why

you can not draw a

straight line graph this time.

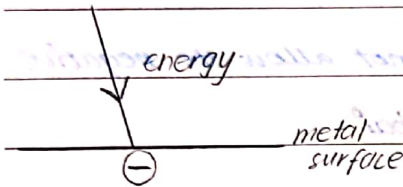


→ the free electron absorbs the energy to overcome the forces of attraction of the metal — if the energy is enough

→ since heat is a form of energy, there is a possibility of electron overcoming attracting the attractive forces if heat is provided the metal surface

→ in both cases there is a possibility b/c we're not sure what exact amount of heat/energy we require

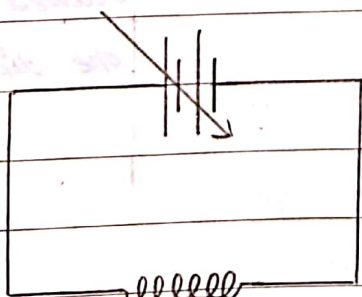thermionic immission: a process in which electron come out of metal when heat is provided to it



* filament offers resistance

* current loses energy to overcome the resistance (electrical)

* the lost energy converts to heat

* filament produces heat

⊖ ⊖ ⊖ tungsten filament
⊖ ⊖ electrons




Date: 15/9/20

cathode ray: a beam of electrons coming out of tungsten filament due to heat

CATHODE RAY OSCILLOSCOPE (CRO)

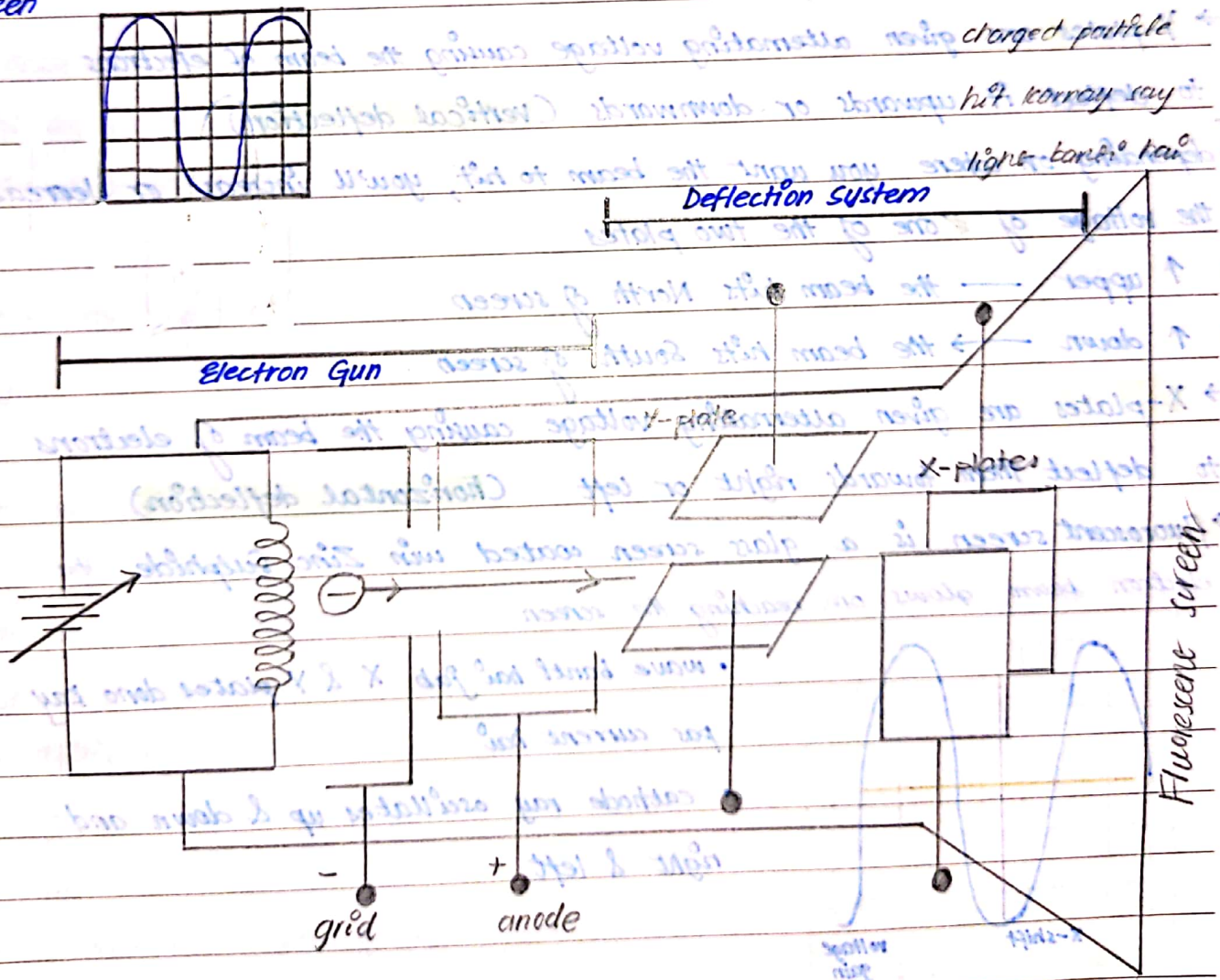→ a device which is used to produce voltage-time trace on the fluorescent screen



Date: 16/9/20

→ parts:

- * electron gun
- * deflection system
- * fluorescent screen

→ electrons overcome the forces of attraction and come outside of the tungsten filament

→ the **grid** helps to form a fine beam of electrons (through repulsion) controls the no. as well

→ the **anode** pulls the electrons and accelerates them

↳ stronger anode — higher speed

→ **Y-plates** are given alternating voltage causing the beam of electrons to deflect it upwards or downwards (**vertical deflection**)


↳ depending on where you want the beam to hit, you'll increase or decrease the voltage of one of the two plates

↳ ↑ upper — the beam hits North of screen

↳ ↑ down — the beam hits South of screen

→ **X-plates** are given alternating voltage causing the beam of electrons to deflect them towards right or left (**horizontal deflection**)

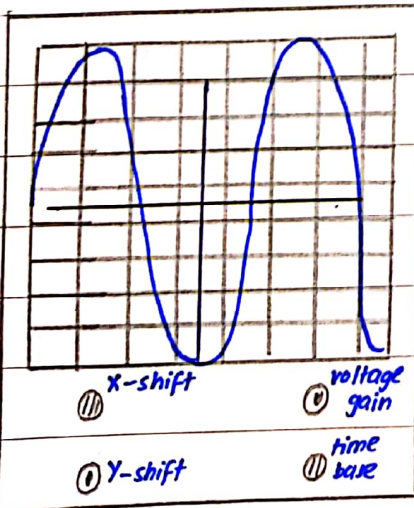→ fluorescent screen is a glass screen coated with Zinc Sulphide, the electron beam glows on reaching the screen



- wave band hai jab X & Y plates dono kay pas current hai
- cathode ray oscillates up & down and right & left



Date: 16/9/20

if only Y plates are given voltage : horizontal line

if only X plates are given voltage : vertical line

to move along X-axis \Rightarrow X-shift button

(the graph)

to move along Y-axis \Rightarrow Y-shift button

Voltage gain : $e.g/5V/cm$

Time base : $e.g/10ms/cm$

voltage = amplitude \times Y-gain

\rightarrow the CRO can be used for :

- * Measuring A.C voltage
- * Displaying voltage waveforms
- * Measuring short intervals of time

voltage sensitivity : it is voltage used by CRO trace per division $e.g/5V/div$

Y-gain

time-base value : it is time used by CRO trace per division $e.g/3ms/div$

**x

\rightarrow the following calculations can be made by using values of voltage sensitivity

and time base :

1). ~~Peak~~ Voltage

(no. of divisions in an amplitude) \times (voltage sensitivity)

2). Time Period

(no. of divisions in one cycle) \times (time base value)

3). Frequency

$$\frac{1}{T}$$



THERMIONIC EMISSION

→ it is emission of electrons from a metal filament, as heated by passing current


→ since, there are large number of free electrons in metals, when current is passed through the metal filament then due to resistance, heating effect is produced

→ the free electrons gain energy and emit out from filament

Deflection by electric field:

* when an electron beam passes b/w two charged plates, it can be observed that the electrons are deflected towards the positive plate

* the electrons are attracted by the positive charges on the positive plates and repelled by the negative charges on the negative plate

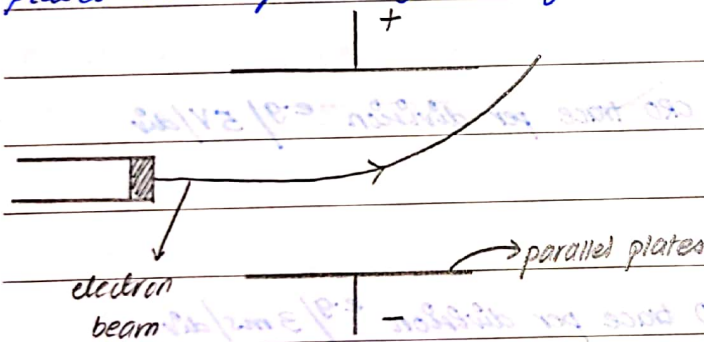**Deflection by magnetic field:**

→ when an electron beam passes b/w two poles of the magnet, it can be observed that the electron beam is deflected

→ using the Left-Hand Rule, it is observed that the beam deflects downwards

