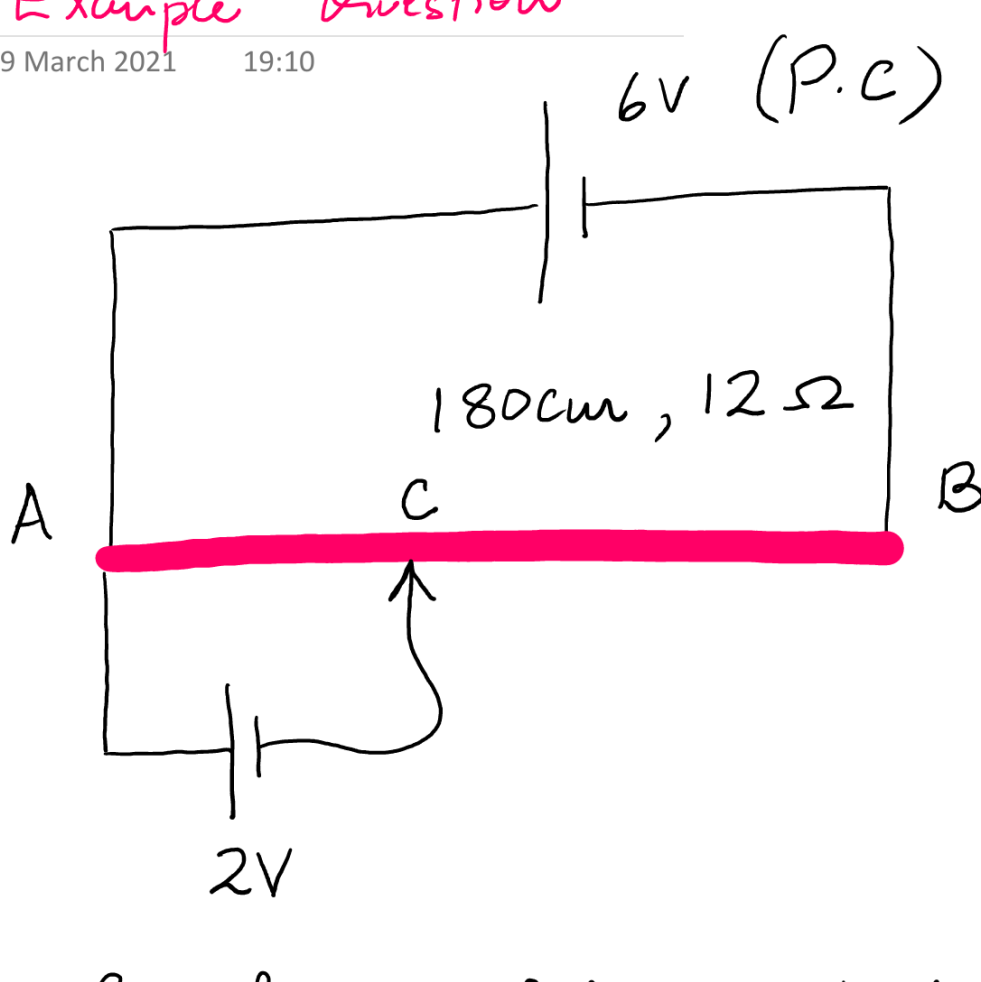


09 March 2021 19:10



(i) Cal. length of AC required to achieve balance point?

Unitary method

General formula

$$180\text{cm} \rightarrow 6\text{V}$$

$$l \leftarrow 2\text{V}$$


$$V = \frac{l_{AC}}{l_{AB}} \times V_{P.C}$$

$$l(AC) = 60\text{cm}$$

$$2 = \frac{l_{AC}}{180} \times 6$$

$$l_{AC} = 60\text{cm}$$

Part (ii)

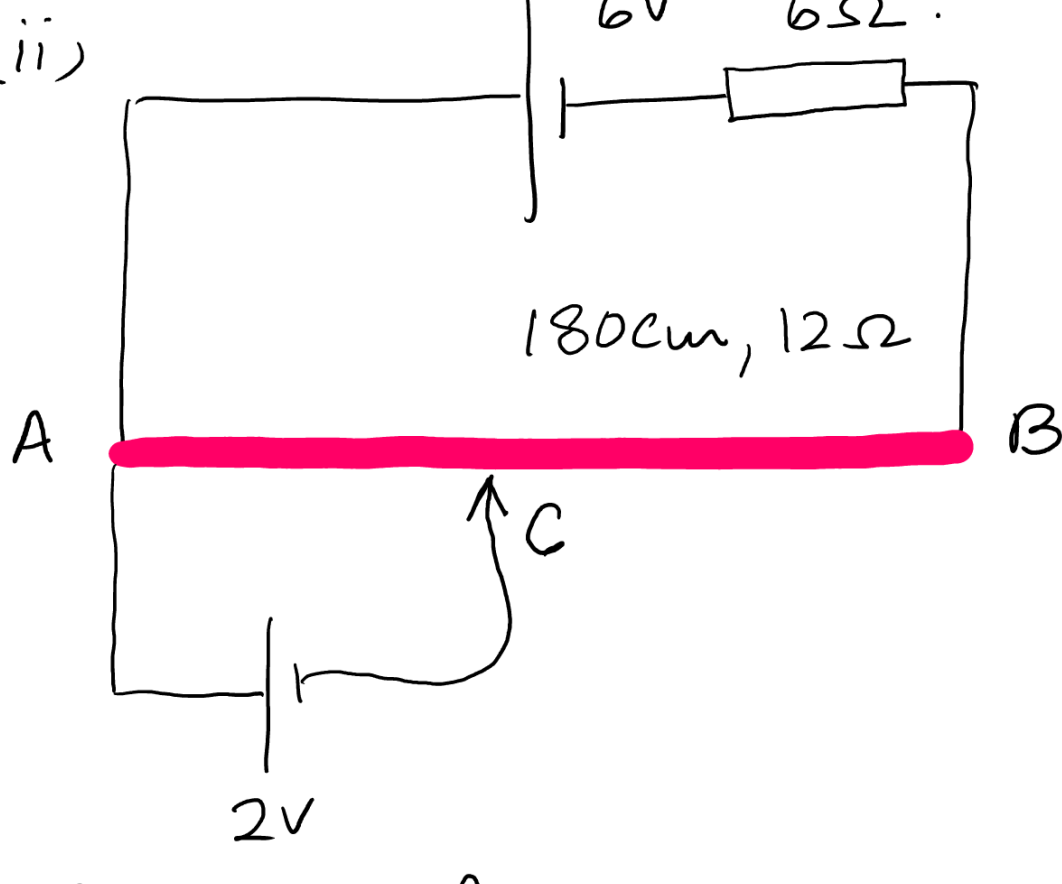

Cal. the new length of AC now required if an additional 6Ω resistor is placed with the Primary cell.

Step 1 Find the voltage now available for the length AB using ratio method

$$\frac{12}{12+6} \times 6 = 4\text{V}$$

$$180\text{cm} \rightarrow 4\text{V}$$

$$l \leftarrow 2\text{V}$$


$$l = 90\text{cm}$$

Conclusion: ∴ If an extra Resistor is placed in the Primary circuit as shown, it causes the length of balance point to **increase**.

Q Give an explanation as to why the length of the balance pt has increased i.e from (60cm → 90cm)

Ans: ∴ If an additional Resistor is placed in the P. Circuit, the voltage **NOW AVAILABLE** for the Resistance wire (AB) reduces ∴ for the same voltage of Secondary cell a much longer length is now required to achieve a balance pt.

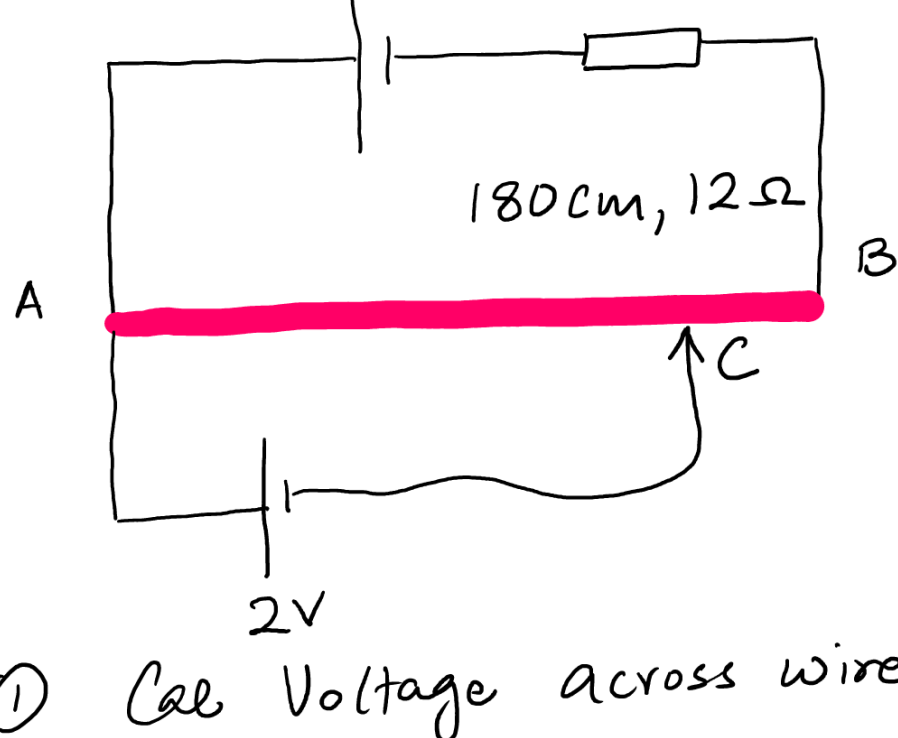Q ∴ What happens if 6Ω resistor is replaced by an 8Ω Resistor?



Step 1 Cal Voltage across wire AB


$$V_{AB} = \frac{12}{12+8} \times 6 = 3.6\text{V}$$

$$\text{Step 2 } 180\text{cm} \rightarrow 3.6\text{V}$$

$$l \leftarrow 2\text{V}$$

$$l_{AC} = 100\text{cm}$$

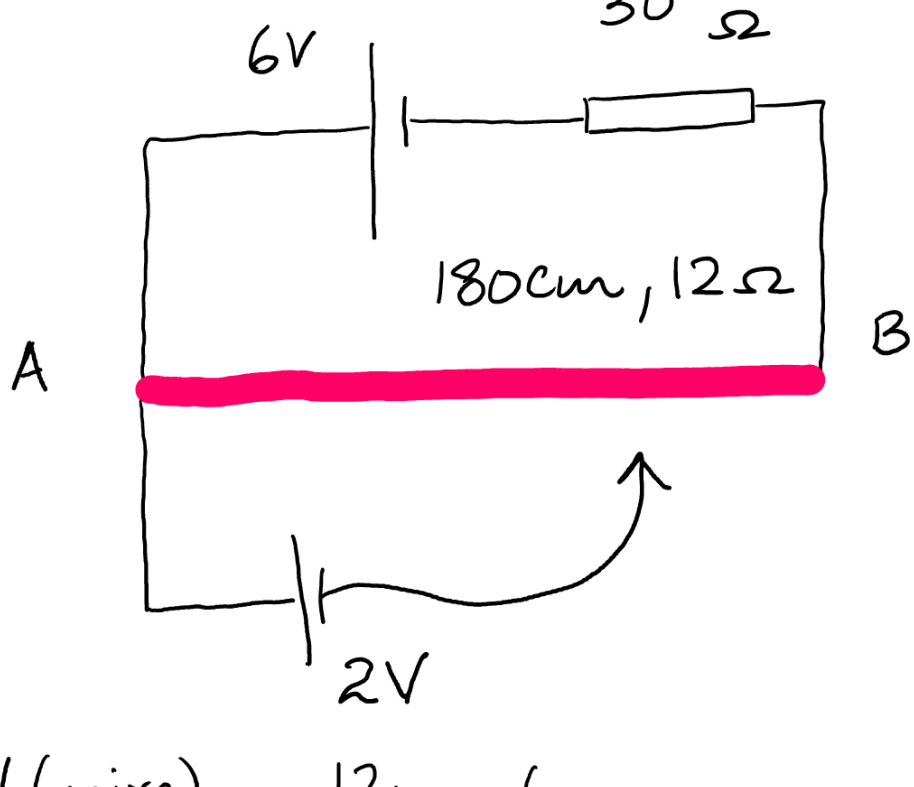Q ∴ What happens if 6Ω resistor gets replaced with a 30Ω resistor.



$$V(\text{wire}) = \frac{12}{12+30} \times 6$$

$$V_{\text{wire}} = 1.71\text{V}$$

No possibility of achieving Balancing point in this case

Conclusion: ∴ Certain Rules must be kept in mind for a Potentiometer circuit to work properly


Rule 1 +ve terminal of the P.C must be connected to the +ve terminal of the Secondary cell.

Rule 2 Voltage of the Secondary Cell must be less than or equal to the voltage available for the wire.

Example Question

09 March 2021

19:37

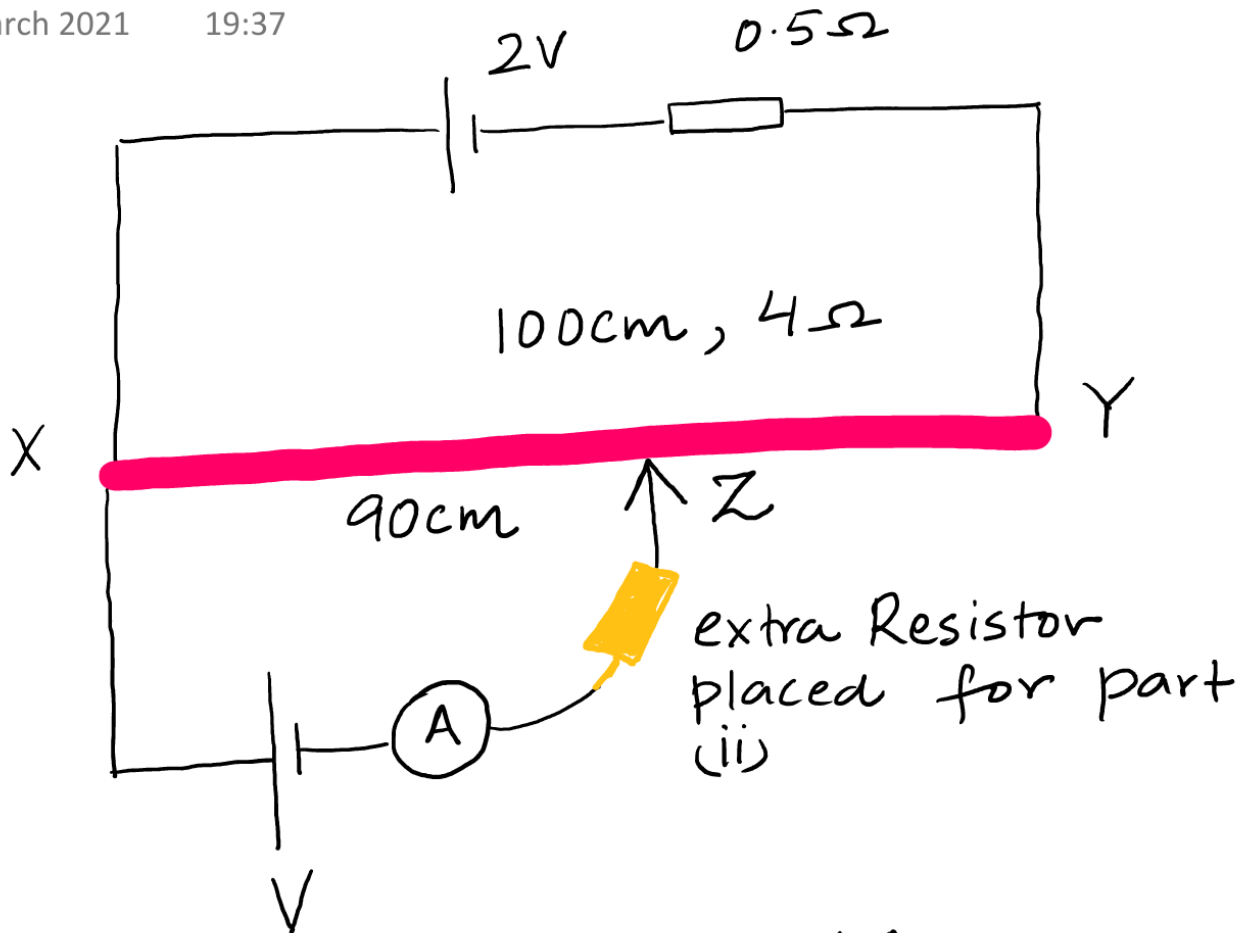

- (i) If that A reads 0A (null deflection). Calculate the unknown voltage V?

Ans $V_{(XY)} = \frac{4}{4+0.5} \times 2 = 1.78V$ step ①

Step ② $100\text{cm} \rightarrow 1.78V$
 $\therefore 90\text{cm} \rightarrow V$
 $V = 1.6V$

- (ii) Suggest why placing an extra resistor in the secondary circuit as shown will not have any effect on the balance pt.

Ans :: The term balance pt indicates that there is Zero Current in the Secondary circuit. Hence even if you place a resistor, based on $V = IR$ the voltage across this resistor will be $V = 0(R)$ i.e. 0V \therefore it will not consume / develop any voltage across itself hence its presence or absence does not affect the Length of the balance point.